

# Robust I2C slave without a sampling clock

25 Aug 2011

I2C is a popular two-wire serial bus protocol for communicating between devices. Most MCUs support it, so it's a good choice of interface for many chips. This article shows how to implement an I2C slave interface without the use of a bus sampling clock.


Bus sampling is a simple way to implement an I2C slave, but in order to support reasonable I2C transfer rates, you need a sampling clock frequency of several MHz. This is fine if the rest of your device already needs such a fast clock, but if it doesn't, then power consumption is needlessly increased. A robust I2C slave can be implemented using nothing but the bus signals for clocking. This has the advantage that the slave interface consumes no power (save for leakage currents) when the bus is idle.

The scheme described here can support any bus speed and is highly reliable. It's compatible with multi-master buses, and doesn't require the master support delayed acknowledgement or clock-stretching.
 
## Overview of the I2C protocol


The I2C bus consists of two lines: `SCL` (serial clock) and `SDA` (serial data), both of which are normally held at logic high via a weak pull-up resistor. Devices control the bus by choosing to pull lines to logic low, or leaving their outputs high-impedance. This is the basic mechanism behind multi-master arbitration, but this won't be covered here -- for simplicity, we'll assume a single master with multiple slaves.

There are three special events generated by the master, called `START`, `STOP` and `RESTART`. These are used, respectively, to begin a transaction, end a transaction, and start a new transaction without releasing control of the bus. Timing diagrams for these three events are shown here:



Timing of the three special control events generated by a master on an I2C bus

 There are two types of byte transfer events: master-to-slave and slave-to-master. The timing for both is the same:



Timing of data transfers on the I2C bus

Data bits are placed on `SDA` MSB-first. In a master-to-slave transaction, the master clocks out a data byte over the first 8 cycles, and then the slave acknowledges on the 9th cycle by pulling `SDA` low. A slave-to-master transaction is exactly the reverse, except that the master only acknowledges if it wishes the slave to transmit another byte. Without this rule, the slave might continue to pull `SDA` down for the next cycle, preventing the master from being able to generate a `RESTART` or a `STOP` event.

The master controls `SCL` (except in the case of clock stretching, which isn't covered here). `SDA` may only change while `SCL` is low, except when the master is generating a `START/RESTART/STOP` event.

## Transaction structure

All transactions begin, after a `START` or `RESTART` event, with a master-to-slave transfer containing an address byte. The upper 7 bits of the address byte are the slave address, and the LSB is the `R/W#` bit, which signifies the direction of the following transfers (low for master-to-slave, high for slave-to-master). If the slave address is recognised by a device on the bus, it acknowledges on the 9th `SCL` pulse by pulling `SDA` low. Other devices must ignore the remainder of the transaction. The transaction ends with a `RESTART` or `STOP` event.

## Typical use

Most slave devices have a number of indexed internal registers. The way I2C is usually used to manipulate the internal registers of such devices is described here. To write a register, the master initiates a write transaction to the desired device. The register index is transferred following the device address, and then the desired data. For example, to write 0x57 to register 3 of device 1010101x, the following sequence of events occurs:

- `START`
- Master-to-slave: device address, `R/W#` = 0 (0xAA)
- Master-to-slave: register index (0x03)
- Master-to-slave: register data (0x57)
- `STOP`

Read transactions are slightly more complex. Since I2C transactions are unidirectional, two transactions are needed, divided by a `RESTART`. The first (write transaction) sends the register index to the device, and the value is sent in the next transaction (read). For example, to read back the value written in the previous example, the following sequence of bus events occurs:

- `START`
- Master-to-slave: device address, `R/W#` = 0 (0xAA)
- Master-to-slave: register index (0x03)
- `RESTART`
- Master-to-slave: device address, `R/W#` = 1 (0xAB)
- Slave-to-master (not acked): register data (0x57)
- `STOP`

Two conventions are usually adopted to make this system more convenient:

- The internal register index is incremented after each transfer. This allows efficient bulk transfer of a block of data to/from logically contiguous registers.
- The internal register index is reset to 0 following a `START` event (but not `RESTART`). Typically, register 0 is a status register, so this allows efficient polling of the status register with a single I2C transaction.

The implementation described in this article follows this conventional scheme.


## Implementation

For this implementation, we will assume an asynchronous reset input, though this won't be shown in circuit diagrams. There is an `SCL` input, and a tri-state `SDA` port. Other interfaces are not covered explicitly.

The flip-flops will be driven mostly by `SCL`. Input data latching must be done on the rising edge, as this is the only time we can guarantee stable data. Conversely, output latching must be done on the falling edge of `SCL`. Internal logic may operate on any edge, but here we use the falling edge consistently.

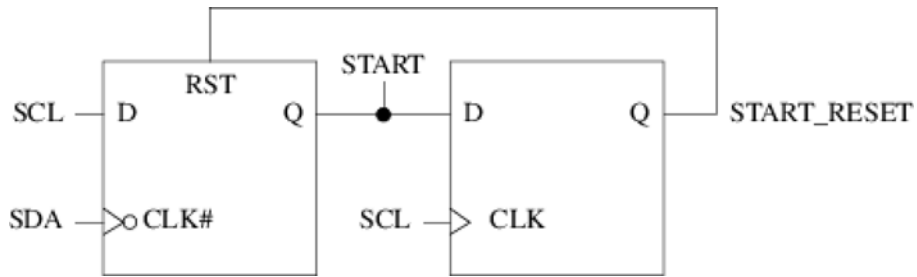
## START/STOP/RESTART

First, we need to be able to detect a `START` event. The following pair of flip-flops will do that:



A `START` detector implemented using a pair of flip-flops.

 This generates a pulse lasting from the `START` event itself to the next rise of `SCL` (covering exactly one falling edge) as shown in the timing diagram:



`START` detector timing.


The Verilog implementation of this is:

```
reg          start_detect;
reg          start_resetter;
wire         start_rst = RST | start_resetter;

always @ (posedge start_rst or negedge SDA)
begin
    if (start_rst)
        start_detect <= 1'b0;
    else
        start_detect <= SCL;
end


always @ (posedge RST or posedge SCL)
begin
    if (RST)
        start_resetter <= 1'b0;
    else
        start_resetter <= start_detect;
end
```

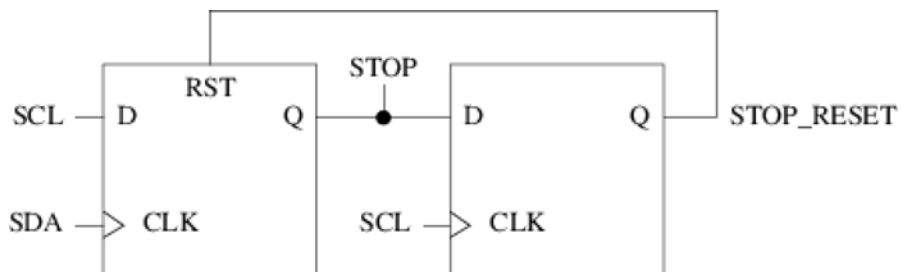The `STOP` detector is similar, except for the sense of the `SDA` clock input:



A `STOP` detector implemented using a pair of flip-flops.

 It generates a pulse from the `STOP` event to the next rise of `SCL`, again covering exactly one fall of `SCL` in the next transaction:



STOP detector timing.

The Verilog implementation is:

```
reg                stop_detect;
reg                stop_resetter;
wire               stop_rst = RST | stop_resetter;

always @ (posedge stop_rst or posedge SDA)
begin
    if (stop_rst)
        stop_detect <= 1'b0;
    else
        stop_detect <= SCL;
end

always @ (posedge RST or posedge SCL)
begin
    if (RST)
        stop_resetter <= 1'b0;
    else
        stop_resetter <= stop_detect;
end
```

Given these two detectors, we don't need to implement a `RESTART` detector -- we can distinguish between a `START` and a `RESTART` by checking to see if a `STOP` event has occurred prior to the `START/RESTART`. Of course, the first `START` after reset will be misinterpreted as a `RESTART`, but in practice this doesn't matter, since we will reset the index pointer on reset anyway.

## Latching input data

To keep track of what stage a transfer is in, we need a modulo-9 counter. It needs to be triggered on the falling edge of SCL, so that it can reset with `START` events:

```
reg [3:0]          bit_counter;

wire               lsb_bit = (bit_counter == 4'h7) && !start_detect;
wire               ack_bit = (bit_counter == 4'h8) && !start_detect;

always @ (negedge SCL)
begin
    if (ack_bit || start_detect)
        bit_counter <= 4'h0;
    else
        bit_counter <= bit_counter + 4'h1;
end
```

We need to latch data bits into a shift register as they appear:

```
reg [7:0]          input_shift;

parameter [6:0]    device_address = 7'h55;
wire               address_detect = (input_shift[7:1] == device_address);
wire               read_write_bit = input_shift[0];

always @ (posedge SCL)
    if (!ack_bit)
        input_shift <= {input_shift[6:0], SDA};
```

Not shifting on the ACK bit means that the data is complete and stable for two clock cycles, which is useful later. Note that since the data is shifted on the positive edge of SCL, we have a complete data byte for two


falling edges of `SCL` -- once with `lsb_bit` high, and once with `ack_bit` high. We need a separate means of detecting acknowledgement during a slave-to-master transfer:

```
reg                master_ack;

always @ (posedge SCL)
    if (ack_bit)
        master_ack <= ~SDA;
```
 
## State machine

Having constructed input handling logic, we can now use it to control a state machine. This machine's states remain stable over an entire transfer, changing at the boundary between transfers, or between transfers and special events. The state transition diagram is:



Transition diagram for I2C slave state machine.

The occurrence of a `START` condition acts as a state machine synchronous reset:

```
parameter [2:0] STATE_IDLE      = 3'h0,
                STATE_DEV_ADDR  = 3'h1,
                STATE_READ      = 3'h2,
                STATE_IDX_PTR   = 3'h3,
                STATE_WRITE     = 3'h4;

reg [2:0]      state;
wire          write_strobe = (state == STATE_WRITE) && ack_bit;

always @ (posedge RST or negedge SCL)
begin
    if (RST)
        state <= STATE_IDLE;
    else if (start_detect)
        state <= STATE_DEV_ADDR;
    else if (ack_bit)
        begin
            case (state)
                STATE_IDLE:
                    state <= STATE_IDLE;

                STATE_DEV_ADDR:
                    if (!address_detect)
                        state <= STATE_IDLE;
                    else if (read_write_bit)
                        state <= STATE_READ;
                    else
                        state <= STATE_IDX_PTR;

                STATE_READ:
                    if (master_ack)
                        state <= STATE_READ;
                    else

```

```

state <= STATE_IDLE;

STATE_IDX_PTR:
    state <= STATE_WRITE;

STATE_WRITE:
    state <= STATE_WRITE;
endcase
end
end

```

## Register transfers

Before handling register transfers, we need to maintain the state of the index pointer. This index is loaded by the first transfer in a write transaction, incremented every other transfer, and reset on a `START` condition (but not `RESTART`). It is implemented as follows:

```

always @ (posedge RST or negedge SCL)
begin
    if (RST)
        index_pointer <= 8'h00;
    else if (stop_detect)
        index_pointer <= 8'h00;
    else if (ack_bit)
        begin
            if (state == STATE_IDX_PTR)
                index_pointer <= input_shift;
            else
                index_pointer <= index_pointer + 8'h01;
            end
        end
end
end

```

Handling register writes is straight-forward. For each register, once per transfer, we check to see if it's being addressed for writing, and if so, we latch the value in the input shift register. For example, to handle writes to a register that has index 0x03:

```

reg [7:0]      reg_03;

always @ (posedge RST or negedge SCL)
begin
    if (RST)
        reg_03 <= 8'h00;
    else if (write_strobe && (index_pointer == 8'h03))
        reg_03 <= input_shift;
    end
end

```

To handle read requests, it's most convenient internally to deal with byte transfers. In order to do this, we need an output shift register. It must be loaded **before** the ACK bit, in order to be ready for the output stage:

```

reg [7:0]      output_shift;

always @ (negedge SCL)
begin
    if (lsb_bit)
        begin
            case (index_pointer)
                8'h00: output_shift <= reg_00;
                8'h01: output_shift <= reg_01;
                // ... and so on ...
            endcase
        end
    else
        output_shift <= {output_shift[6:0], 1'b0};
    end
end

```

## Output driver

Finally, we're ready to implement the output driver. We latch the output driver control signal to prevent bus glitches. The signal switches the driver between two states: high-impedance and pull-low. We pull low only under the following circumstances:

- Acknowledging an address.
- Acknowledging a master-to-slave transfer.
- Transmitting a zero during a slave-to-master transfer.

The logic is a little subtle, because we have to set the state for the **next** SCL clock cycle, taking into account that the state machine's state for the next cycle may not be the same as what it is for the current cycle (note in particular the logic for delivering the first bit of the first transfer in a read transaction):

```
reg          output_control;
assign      SDA = output_control ? 1'bz : 1'b0;

always @ (posedge RST or negedge SCL)
begin
    if (RST)
        output_control <= 1'b1;
    else if (start_detect)
        output_control <= 1'b1;
    else if (lsb_bit)
        begin
            output_control <=
                !(((state == STATE_DEV_ADDR) && address_detect) ||
                  (state == STATE_IDX_PTR) ||
                  (state == STATE_WRITE)));
        end
    else if (ack_bit)
        begin
            // Deliver the first bit of the next slave-to-master
            // transfer, if applicable.
            if (((state == STATE_READ) && master_ack) ||
                ((state == STATE_DEV_ADDR) &&
                 address_detect && read_write_bit))
                output_control <= output_shift[7];
            else
                output_control <= 1'b1;
        end
    else if (state == STATE_READ)
        output_control <= output_shift[7];
    else
        output_control <= 1'b1;
end
```

## Synchronization

It's unlikely that a device will be clocked solely by SCL. There will probably be other internal clock domains, and the I2C interface must be able to transfer data to and from these domains.

A two-phase REQ/ACK scheme is unsuitable in most cases due to the intermittent clock driving the I2C interface. However, since the device is likely being addressed by an MCU, software assistance on the part of the master can make the task easier.

### Write synchronization

Provided data is not written more than once every few cycles of the other clock domain, a single-phase synchronization scheme is feasible. For each writable piece of data which must be synchronized, implement a data phase bit. Whenever the register is written, toggle the data phase register.

In the other clock domain, the data phase bit is sampled through a two-flop synchronizer. When a change is detected in the sampled data phase signal, the data in the I2C slave interface register can be latched into a register in the other clock domain.

This general scheme is fairly flexible, but other schemes may be possible, depending on the application. One simple scheme is to designate one bit in an I2C interface register to be an asynchronous reset for logic in the other domain, and require that software only change configuration registers while this reset is asserted.

### Read synchronization

Since there is no minimum speed for I2C transfers, a data-phase toggle scheme as described above can't be guaranteed to work correctly for reads. Instead, negotiation is required between the MCU and the internal logic via the I2C interface.

For example, one control bit in an I2C register may be designated a "read-request" bit. This could trigger the internal logic to update the data presented and set a "read-ready" bit. The read-ready bit can be sampled through a two-flop synchronizer driven by `SCL` (this is always possible for single bits). By the time the device has been addressed, the state of the synchronized read-ready bit should be up to date. At this point, the MCU can check the sampled bit and then decide whether it's possible to read the appropriate data register.

This scheme is a natural fit to reading the results of "one-shot" tasks. In many cases, the MCU will request a task to be executed by means of a control bit. It can then poll a status bit to be notified of task completion (with associated return data).